

Reg. No.: _____

Amrita Vishwa Vidyapeetham

Amrita School of Engineering, Bengaluru

B.Tech. Missed Mid Term Exam – December- 2023

Electrical and Electronics Engineering

First Semester CSE (A, B, C)

23EEE104 Introduction to Electrical and Electronics Engineering

Time: Two hours

Maximum marks: 50

CO	Course Outcomes
CO1	Ability to understand the basic electric and magnetic circuits.
CO2	Ability to analyse DC and AC circuits.
CO3	Ability to understand the basic principles of pn junctions and transistors.
CO4	Ability to analyse basic transistor and opamp based circuits

Answer all questions

Find the form factor for the given waveform of Fig. 1.

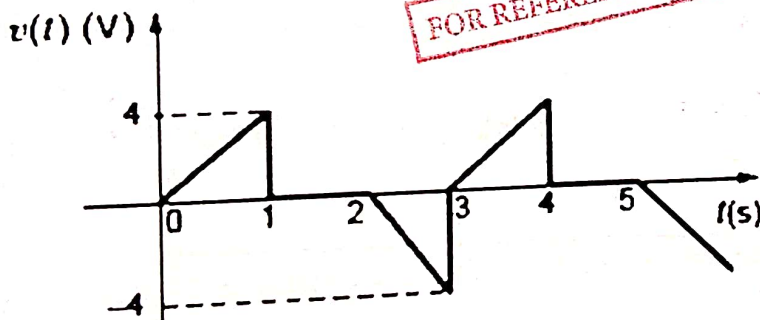
[6] CO2
BTL3

Fig. 1

Find the power dissipated in 8 ohm resistor of the circuit shown in Fig.2 using super position theorem

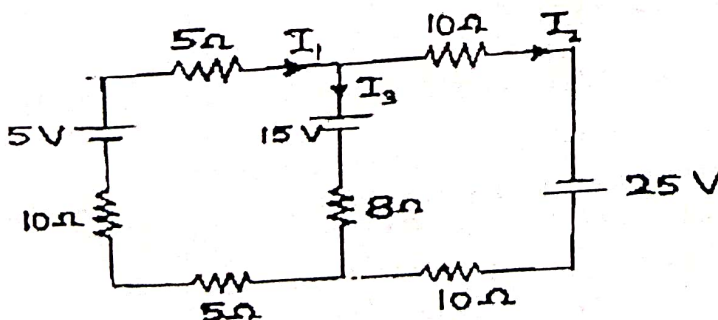
[10] CO2
BTL3

Fig.2

Three capacitors of values $8\mu\text{F}$, $12\mu\text{F}$ and $16\mu\text{F}$ respectively are connected in series across a 240 V DC supply. Calculate (i) the resultant capacitance and (ii) p.d. across each capacitor (iii) energy stored by each capacitor[8] CO1
BTL2

19

4

For the given network in Fig.3 Find the equivalent inductance across AB

[3]

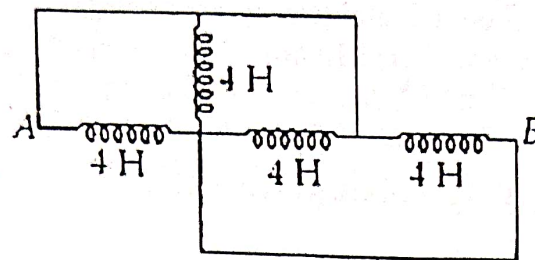


Fig.3

5

An air cored solenoid with a diameter of 1.2 cm and a mean length of 8 cm is wound uniformly with 500 turns. If a current of 10 A flows through the coil. Find the (i) Magneto motive force (ii) reluctance of the ring (iii) flux (iv) inductance and (v) induced emf, if the flux falls to zero in 10 ms .

[7]

6

Find the power dissipated through $2\text{ k}\Omega$ resistor in the circuit shown in Fig. 4 using nodal analysis.

[8]

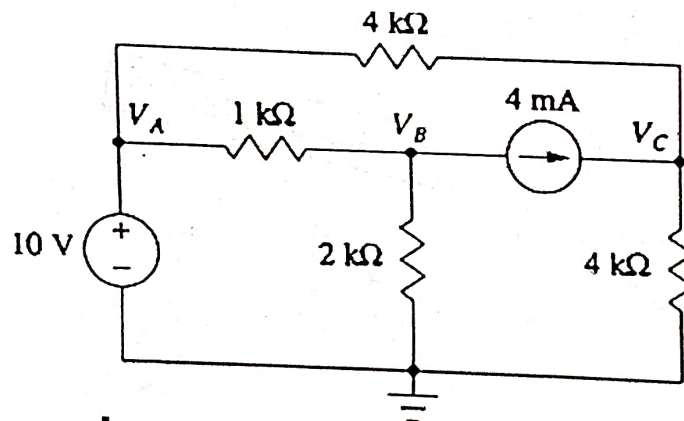


Fig. 4

7.

A resistance of 50Ω and an inductor of 50 mH are connected in series. If an alternating voltage of 100 V at 50 Hz frequency is applied across it, find the current, active power, reactive power and apparent power and the power factor. Draw the phasor diagram.

[8]

Course Outcome / Bloom's Taxonomy Level (BTL) Mark Distribution Table

CO	Marks	BTL	Marks
CO1	18	BTL 1	-
CO2	32	BTL 2	19
CO3	-	BTL3	31
CO4	-	-	-