

Amrita Vishwa Vidyapeetham  
Amrita School of Engineering, Bengaluru  
B.Tech. Mid Term Exam – Oct. 2023  
Electrical and Electronics Engineering  
First Semester(CSE A, B, C)

23EEE104 Introduction to Electrical and Electronics Engineering

Time: Two hours

Maximum marks: 50

CO	Course Outcomes
CO1	Ability to understand the basic electric and magnetic circuits.
CO2	Ability to analyse DC and AC circuits.
CO3	Ability to understand the basic principles of pn junctions and transistors.
CO4	Ability to analyse basic transistor and opamp based circuits

Answer all questions

Find the equivalent resistance  $R_{AB}$  using network reduction method from Fig. 1. [5] CO1 BTL3

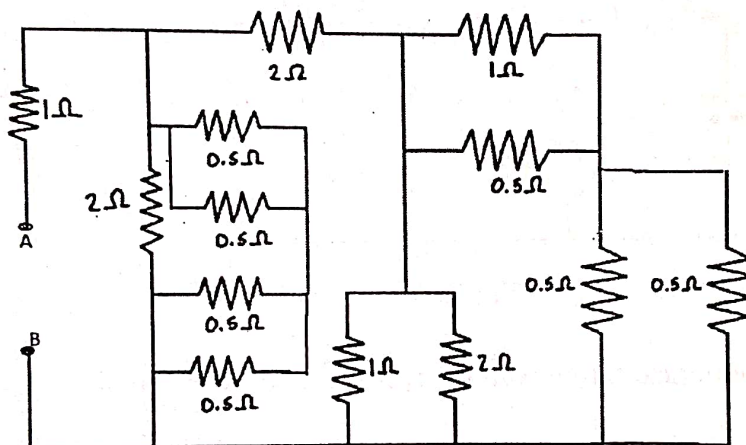


Fig. 1

A flux of  $0.6\text{mWb}$  is created by a current of  $12\text{A}$  flowing through a  $120$  turn coil. Calculate the inductance of the coil corresponding to the complete reversal of the current in  $0.02\text{s}$ . Also find magnitude of the induced emf. [5] CO1 BTL2

Three capacitors A, B and C are connected in series across a  $200\text{V}$  DC supply. The potential difference across them are  $40\text{V}$ ,  $70\text{V}$  and  $90\text{V}$  respectively. If the capacitance of the capacitor B is  $70\mu\text{F}$ , find the values of the capacitance of the capacitor A and capacitance of the capacitor C. [5] CO1 BTL3

Draw the schematic representations of ideal and practical independent voltage source. [4] CO1 BTL1

For the circuit shown in Fig. 2, calculate the current through  $6\Omega$  resistor and total current. [6] CO2 BTL3

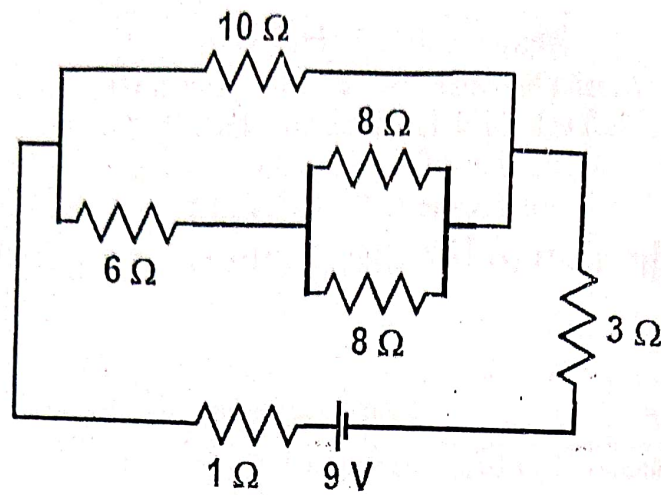


Fig. 2

- 6 Find the currents through all the resistors of the circuit shown in Fig. 3, using mesh analysis. [10]

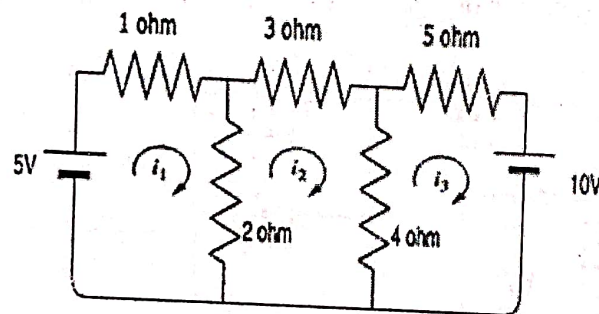


Fig. 3

- 4 Find the power dissipated through all the resistors shown in Fig. 4 using nodal analysis. [10] C B1

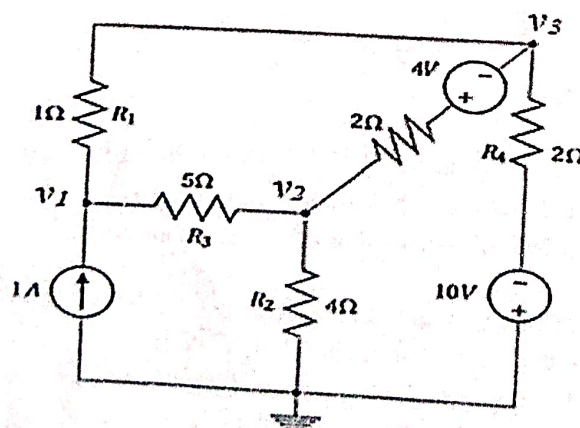


Fig. 4

- 6 Find the equivalent capacitance from the circuit shown in Fig. 5. [5] CO1 BTL3

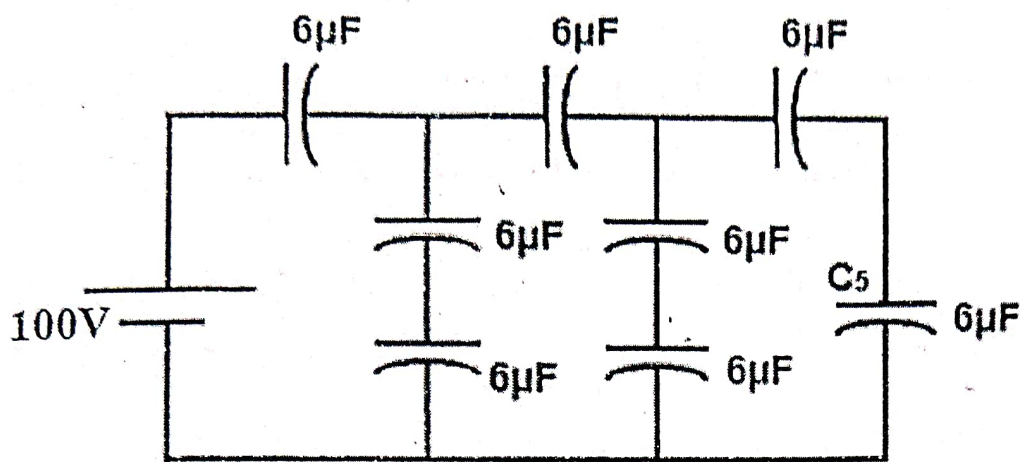


Fig. 5

**Course Outcome / Bloom's Taxonomy Level (BTL) Mark Distribution Table**

CO	Marks	BTL	Marks
CO1	24	BTL 1	04
CO2	26	BTL 2	05
CO3	-----	BTL 3	41
CO4	-----	-----	-----

FOR REFERENCE ONLY